

**ΘΕΜΑ Α**

**Α.1.**


1. → .δ.
2. → .α
3. → .γ
4. → .δ
5. → .γ

**ΘΕΜΑ Β**


**Β.1**

1. → .δ
2. → .α
3. → .β
4. → .ε

**Β2.**

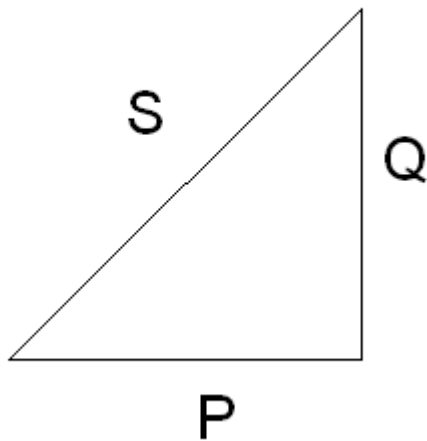

α. Επαγωγική  
Συμπεριφορά

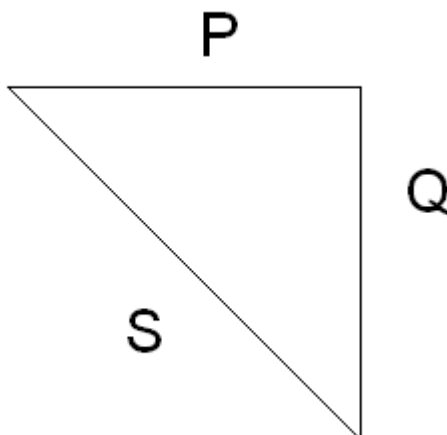

β. Χωρητική  
Συμπεριφορά

**B.3**

$$\frac{\pi}{4} + \omega \cdot t = \frac{\pi}{4} + 2 \cdot \pi \cdot f \cdot t = \frac{\pi}{4} + 2\pi \cdot 50 \cdot 0,01 = \frac{\pi}{4} + \pi \cdot 100 \cdot 0,01 =$$

$$\frac{\pi}{4} + \pi = \frac{\pi}{4} + \frac{4\pi}{4} = \frac{\pi + 4\pi}{4} = \frac{5\pi}{4} = \frac{5\pi}{4}$$

ή

$$45^\circ + \omega t = 45^\circ + 2 \cdot \pi f t = 45^\circ + 2 \cdot 180^\circ \cdot 50 \cdot 0,01 = 180^\circ \cdot 100 \cdot 0,01 = 45^\circ + 180^\circ = 225^\circ$$

**ΘΕΜΑ Γ**

$$\Gamma 1. U_R = I \cdot R = 2 \cdot 3 = 6\Omega$$

$$\Gamma 2. R_{o\lambda} = R + R_\pi = 3 + 1 = 4\Omega$$

$$\Gamma 3. Z = \sqrt{R_{o\lambda}^2 + X_L^2} = \sqrt{3^2 + 4^2} = \sqrt{9^2 + 16^2} = \sqrt{25} = 5\Omega$$

$$\Gamma 4. \sigma \nu \phi = \frac{R_{o\lambda}}{Z} = \frac{4}{5} = 0,8$$

~

$$\Gamma 5. U = Z \cdot I = 5 \cdot 2 = 10V$$

$$P = U \cdot I \cdot \sigma \nu \phi = 10 \cdot 2 \cdot 0,8 = 16W$$

**ΘΕΜΑ Δ**

$$\Delta 1. U_\phi = 660V$$

$$\Delta 2. I_\phi = \frac{U_\pi}{R} = \frac{660}{30} = 22A$$

$$\Delta 3. I_{\gamma\rho} = \sqrt{3} \cdot I_\phi = \sqrt{3} \cdot 22..A$$

$$\Delta 4. P_{ολ} = \sqrt{3} \cdot U_{πολ} \cdot I_{γρ} \cdot \sigma\upsilon\nu\phi = \sqrt{3} \cdot 660 \cdot 22 \cdot \sqrt{3} \cdot 1 = 45560W$$

Δ5. Η ολική αντίσταση του φορτίου, τώρα, είναι:

$$R_{ολ} = \frac{R \cdot (R + R)}{R + (R + R)} = \frac{R \cdot 2R}{R + 2R} = \frac{2R^2}{3R} = \frac{2R}{3} = \frac{2 \cdot 30}{3} = 20 \Omega$$

$$I' = \frac{U_{πολ}}{R_{ολ}} = \frac{660}{20} = 33 \text{ A}$$

Άρα η νέα ισχύς, είναι:

$$P' = U_{πολ} \cdot I' \cdot \sigma\upsilon\nu\phi = 660 \cdot 33 \cdot 1 = 27780 \text{ W}$$